

13/7/13

--	--	--	--	--	--	--	--

B.E Full Time Degree END SEMESTER EXAMINATIONS, April/May 2013

Fifth Semester, EEE Reg 2008

EE 9303 Linear Integrated Circuits

Time: 3 Hours

Max. Marks: 100

Answer ALL Questions

PART – A (10 x 2 = 20 Marks)

1. What is advantage of digital circuits over analog circuits?
2. List the ideal characteristics of OpAmp.
3. If in a OpAmp IC ,a 0.3 V change in common mode input causes a DC output offset change of 3mV,determine the CMRR in dB.
4. Write briefly on the R-2R ladder type D/A converter for 8421 code conversion.
5. What is the need for converting a Lowpass Filter into a High pass filter?
6. Discuss on a suitable circuit suited to detect the nonsinusoidal input waveform using OpAmp.
7. If V (DC) is 15V, v(ripple: peak to peak) is .25v determine the ripple factor & the percentage ripple.
8. How is frequency division realized in a PLL circuit?
9. What are the need for optocouplers?
10. Distinguish the principle of Linear regulator and a switched mode power supply.

PART – B ( 5 x 16 = 80 Marks)

1. i) Derive the functional parameters for an Inverting mode feedback circuit with OpAmp. ii) How is it better than the non-inverting Amplifiers?  
iii) For a 741 OpAmp IC Inverting mode ,with  $R_1=1\text{Kohm}$ ,  $R_f=2.5\text{ Kohm}$ , compute  $A_f$ ;  $R_{if}$ ;  $R_{of}$ ; BW; offset voltage. (7+2+7)
  12. a. i. What are the advantages of integrating type A/D converters?  
ii. Design a OpAmp based Integrator circuit.  
iii. Discuss on the Integrating type ADC realization using OpAmp. (2 + 7+7)
- (OR)
12. b. i). What are the types of voltage comparator techniques?  
ii). For an open loop inverting mode OpAmp,if  $v_{in} = 2\text{V}$  peak to peak sinewave at 500Hz, supply voltages=12V DC fitted with external pot that changes the  $V(\text{Ref})=0\text{V}; 0.5\text{V}; - .2\text{V}$ . Draw the output waveforms.  
iii). Design & explain a Schmitt Trigger circuit. (2 + 7+7)

- 13.a Design a Sine wave Generator using OpAmp to output a frequency of 3 KHz . with  $C = 0.01 \mu\text{F}$ .  
What is the design attribute in the circuit to obtain a cosine wave generation?  
(10 + 6)

(OR)

- 13.b. Write briefly on any two of the following: (8 + 8)
- Successive Approximation Type A/D converter.
  - Opamps as Comparators
  - Clipper and Clamper circuits.

- 14.a. i) How are Filters categorized?  
ii) Design a Analog First order Low pass Filter using OpAmp.  
iii) Why is the first order Butterworth Low Pass filter converted to second order filter

(2+10+4)

(OR)

- 14.b. Design a Square Wave Generator. Explain how a Triangular Wave ; Sawtooth wave is Generated with this circuit. (8+4+4)

- 15.a. (i) Describe the 555 Timer IC .(ii) Design a Astable Multivibrator Circuit to generate output Pulses of 25%,50% duty cycle using a 555 Timer IC. with choice of  $C=0.1\mu\text{F}$ , Frequency as 3.0KHz .  
(8+8)

(OR)

15. b. Answer any two of the following: (8+8)
- Switched capacitor filters.
  - LM 380 power amplifier.
  - IC Fabrication technique to realize capacitor, Transistor.