

**BE/BTECH (FT-arrear) DEGREE END SEMESTER EXAMINATIONS APR/MAY-2014**  
**DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**  
**III SEMESTER**  
**EC8301 ELECTRONIC CIRCUITS-I**  
**(Regulation 2012)**

Time:3Hrs

Max Marks:100



Answer all questions  
**Part-A (10 X 2=20 Marks)**

- 1) Compare Fixed-bias, Collector-to-base bias and Voltage divider bias of BJT biasing methods.
- 2) Compare between JFET and MOSFET amplifiers
- 3) Calculate the small-signal voltage gain of the bipolar transistor circuit shown in Figure 1. Assume the transistor and circuit parameters are  $\beta=100$ ,  $V_{CC}=12V$ ,  $V_{BE}=0.7V$ ,  $R_C=6k\Omega$ ,  $R_B=50k\Omega$  and  $V_{BB}=1.2V$ .
- 4) Define CMRR of BJT differential amplifier. How to improve it?
- 5) Determine the input impedance of CG amplifier
- 6) Compare Common-Source, Common-Drain and Common-Gate Amplifiers based on their characteristics.
- 7) Compare between NMOS inverter with enhancement, depletion and resistive load
- 8) Draw the small signal circuit diagram of CMOS Common source amplifier
- 9) What is the relationship between  $f_\beta$  and  $f_\alpha$
- 10) Define Miller effect

Part-B (5 X 16=80 Marks)

11) i) Explain Current-steering Circuit in detail (8)

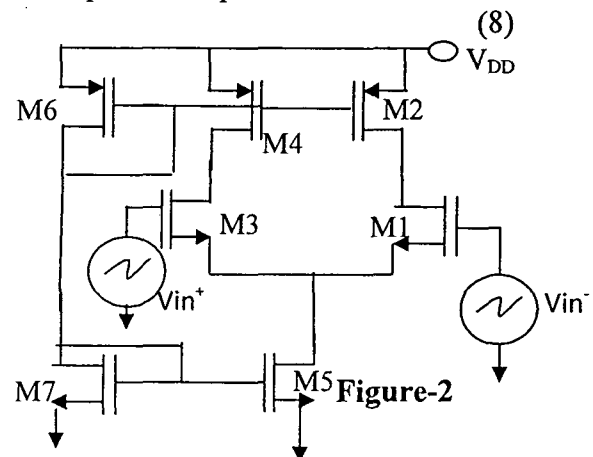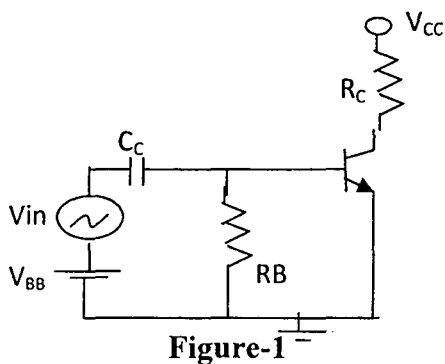ii) Determine the differential voltage gain, common-mode voltage gain and CMRR of the CMOS differential amplifier as shown in Figure 2. The transistor parameters are  $K_n=100\mu A/V^2$ ,  $K_p=50\mu A/V^2$ ,  $V_{tn}=0.8V$ ,  $(W/L)_{NMOS}=15$ ,  $(W/L)_{PMOS}=30$ ,  $V_{tp}=-0.6V$ ,  $I_D=200\mu A$ ,  $\lambda_n=0.01V^{-1}$ ,  $\lambda_p=0.008V^{-1}$  and minimum overdrive voltage of 0.3V is required to operate all transistors in the saturation region. (8)



12)a) Determine the change in collector current produced in each bias referred to in example Figure 3. When the circuit temperature raised from 25°C to 105°C and  $I_{CBO} = 15\text{nA} @ 25^\circ\text{C}$  (16)

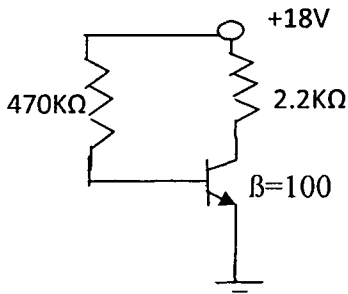


Figure-3(a)

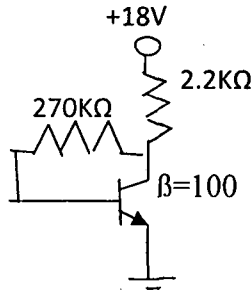


Figure-3(b)

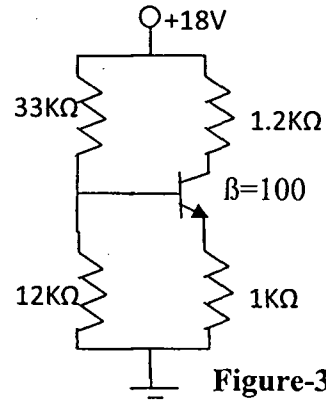


Figure-3(c)

(OR)

b)(i) Calculate the drain current and source-to-drain voltage of a Common-source Circuit with P-channel enhancement mode MOSFET shown in Figure 4. Let  $V_{tp} = -0.8\text{V}$  and  $\beta_p = 0.4\text{mA/V}^2$  (8)

ii) Define and derive the stability factors for BJT self bias (voltage-divider bias) circuit. (8)

13)a) i) For each transistor in the Darlington circuit shown in Figure 5 has the parameters of  $\beta = 100$ ,  $V_A = \infty$ . Determine its overall voltage gain, input impedance and output impedance. (8)

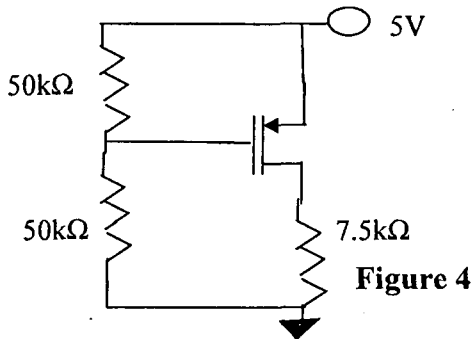


Figure 4

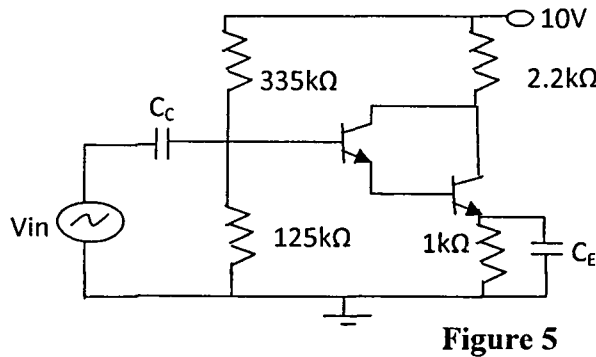


Figure 5

(ii) Determine the small signal voltage gain, input impedance and output impedance of cascode amplifier. (8)

(OR)

b) For the circuit in Figure 6, the parameters are  $R_B = 100\text{k}\Omega$ ,  $R_E = 10\text{k}\Omega$ ,  $R_C = 10\text{k}\Omega$ ,  $V_{CC} = V_{EE} = 10\text{V}$ ,  $R_L = 1\text{k}\Omega$ ,  $R_S = 1\text{k}\Omega$ ,  $\beta = 125$  and  $V_A = \infty$ . (w) Determine the small signal voltage gain (x) Determine small signal current gain (y) Determine the input resistance,  $R_{in}$  (z) Determine the output resistance,  $R_o$ . (16)

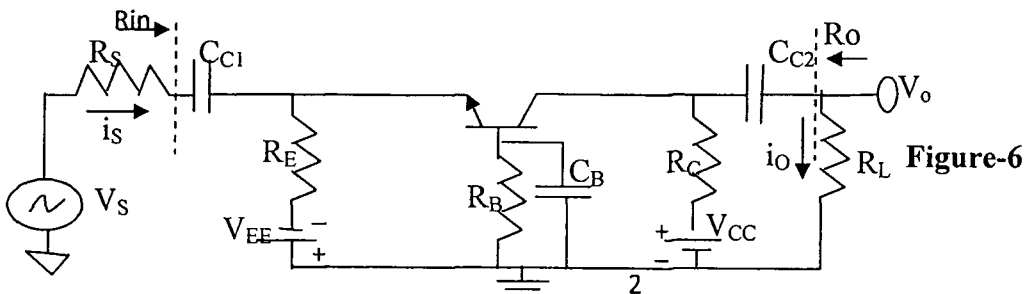


Figure-6

14(a) i) Determine the Voltage gain, input impedance and output impedance of BIMOS amplifier (8)

(ii) Consider the circuit shown in Figure 7 with circuit parameters  $V^+=5V$ ,  $V^-=-5V$ ,  $R_S=4k\Omega$ ,  $R_D=4k\Omega$ ,  $R_L=4k\Omega$  and  $R_G=50k\Omega$ . The transistor parameters are  $V_{tp}=-0.8V$ ,  $\beta_p=2mA/V^2$  and  $\lambda=0$ . Draw the small signal equivalent circuit, determine the small signal voltage gain, input impedance and output impedance. (8)

(OR)

b)i) Determine the voltage gain and input impedance of JFET Common source amplifier (8)

ii) The transistor in the source-follower circuit shown in Figure 8 is biased with a constant current source. The transistor parameters  $V_{tn}=2V$ ,  $K_n=40\mu A/V^2$  and  $\lambda=0.01V^{-1}$ . The load resistor  $R_L=4k\Omega$ . (x) Design the transistor width-to-length ratio such that  $g_m=2mA/V$  when  $I=0.8mA$ . What is the correspondence value for  $V_{GS}$ ? (y) Determine the small-signal voltage gain and output impedance. (8)

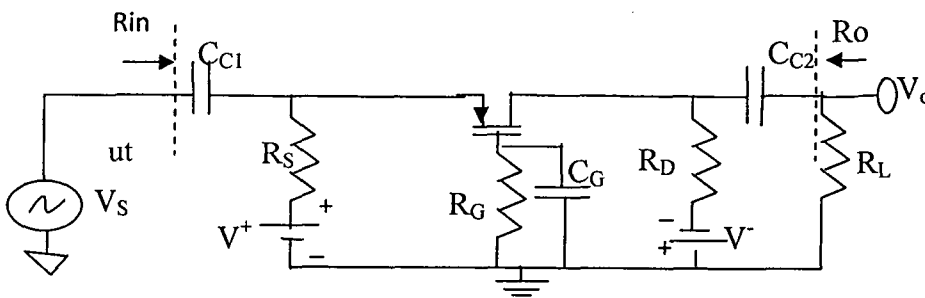


Figure-7

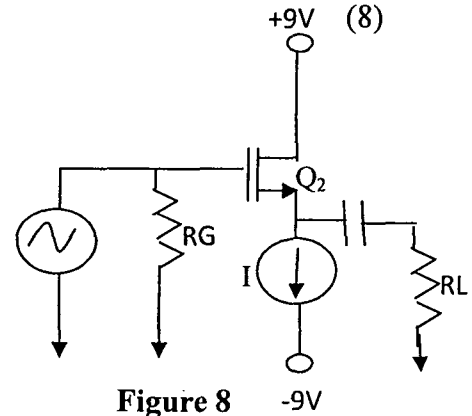


Figure 8

15)a) Determine the Midband gain, Upper Cutoff frequency of a Common-Source amplifier fed with the signal having internal resistance  $R_{sig}=100k\Omega$ . The amplifier has  $R_G=4.7M\Omega$ ,  $R_D=R_L=15k\Omega$ ,  $g_m=1mA/V$ ,  $r_o=150k\Omega$ ,  $C_{gs}=1pF$  and  $C_{gd}=0.4pF$ . Also find the values of  $C_{C1}$ ,  $C_{C2}$  and  $C_S$  by assuming lower cutoff frequency of 100Hz and that the nearest break frequency be atleast a decade lower. (vide Figure 9) (16)

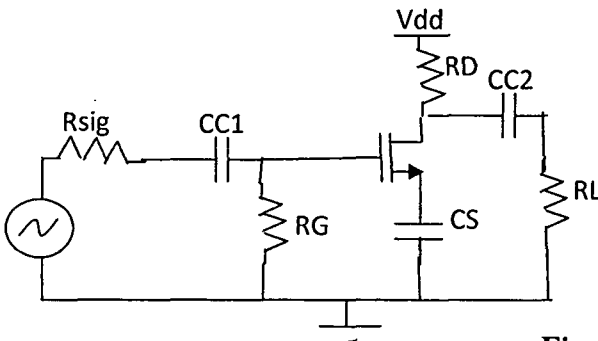


Figure 9

(OR)

b)i) Determine mid-band gain and upper cut-off frequency of Common Emitter amplifier (8)

ii) Determine mid-band gain and upper cut-off frequency of Common Source amplifier (8)