

BE (Regular) Degree End Semester Examinations, April/May 2014
IV Semester
EC8403 Electronic Circuits II
Reg-2012

Total Marks:100
Duration: 3Hrs

Answer All Questions

PART-A (10 X 2 =20 Marks)

- 1) Why single pole system is unconditionally stable?
- 2) Draw a circuit diagram of two stage voltage series feedback amplifier using BJTs and write its expression for feedback factor.
- 3) State Barkhausen criteria for oscillation.
- 4) A ring oscillator is constructed with three inverting amplifiers each with a bandwidth of 10KHz. Find the frequency of oscillation.
- 5) What is use of transformer in tuned amplifier circuit.
- 6) Differentiate between Synchronous and Staggered tuned amplifiers
- 7) List out the features of Chebyshev Filters.
- 8) A second-order filter has its poles as $s = -1/2 \pm j(\sqrt{3}/2)$. The transmission is zero at $\omega = 3\text{rad/s}$ and is unity at dc ($\omega = 0$). Find the transfer function.
- 9) Determine the maximum power dissipation in a transistor.
 $\theta_{\text{dev-case}} = 1.75^\circ\text{C/Watts}$, $\theta_{\text{case-sink}} = 1^\circ\text{C/Watts}$, $\theta_{\text{sink-amb}} = 5^\circ\text{C/Watts}$, $T_{j\text{max}} = 150^\circ\text{C}$ and $T_{\text{amb}} = 30^\circ\text{C}$.
- 10) In Class-A power amplifier the output voltage across the direct coupled load of 10 ohms is $4\sin\omega t$. Let $V_{CC} = 12\text{V}$. Determine its conversion efficiency.

PART-B (5 X 16 =80 Marks)

- 11) i) Design a low-pass filter by using butterworth approximation. Let $f_p = 1\text{KHz}$, $f_s = 1.5\text{KHz}$, $A_{\text{max}} = 1\text{dB}$, $A_{\text{min}} = 50\text{dB}$, dc gain = 1. (8)
 - ii) Explain the principle of switched capacitor filter using inverting integrator (4)
 - iii) Design & Draw the first order high-pass filter with a corner frequency is 10^4 rad/s , and a high frequency gain is 10. Assume $R = 10\text{K}\Omega$ to produce corner frequency. (4)
- 12) a) i) Draw the single stage current series feedback amplifier using BJT. Derive its overall trans-conductance gain, G_{MF} , Input Impedance, R_{if} , Output Impedance R_{of} .
- (ii) Determine the trans-resistance gain R_{MF} , Input Impedance, R_{if} , Output Impedance, R_{of} of single stage voltage shunt feedback amplifier (BJT version).

From their characteristics find the suitable amplifier to amplify the signal-Reason-out why?

(5+5+2)

(iii) An amplifier is given negative feedback to reduce the gain from 10^5 to 50. Find the value of feedback factor. Also find the % change in gain with feedback (dA_f in %) assuming change in gain without feedback is 10% (4)

(OR)

b) i) Consider a three-pole feedback amplifier with a loop gain given by

$$T(f) = \frac{5 \cdot 10^5}{\left(1 + j \frac{f}{10^6}\right) \left(1 + j \frac{f}{10^7}\right) \left(1 + j \frac{f}{10^8}\right)}$$

Determine the

(x) Frequency of the dominant pole to stabilize the feedback system. Assume the phase margin is at least 45° .

(y) The value of the feedback capacitor (to create dominant pole) when the gain of an amplifier is 10^3 and its resistance, R is $0.1 \text{ M}\Omega$. (8)

(ii) Identify the nature of feedback in Figure-1. Let $R_{C1} = 3 \text{ K}\Omega$, $R_{C2} = 500 \Omega$, $R_E = 50 \Omega$, $R_S = R_F = 1.2 \text{ K}\Omega$, $h_{fe} = 50$, $h_{ie} = 1.1 \text{ K}\Omega$, $h_{re} = h_{oe} = 0$. Determine the overall voltage gain (A_{vf}), overall current gain (A_{if}), (8)

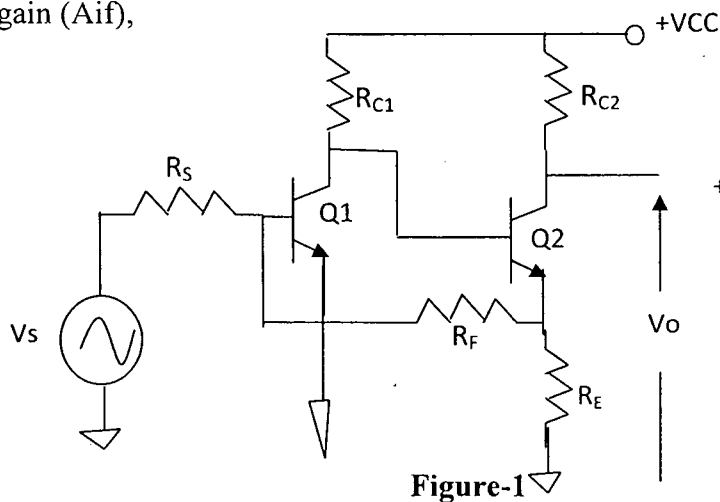


Figure-1

13) a) i) Explain RC-Phase shift oscillator using BJT transistor. Determine its frequency of oscillation. (10)

ii) Design an oscillator with feedback network shown in Figure-2. Let $V_{CC} = 20 \text{ V}$ and $h_{fe} = 150$. (6)

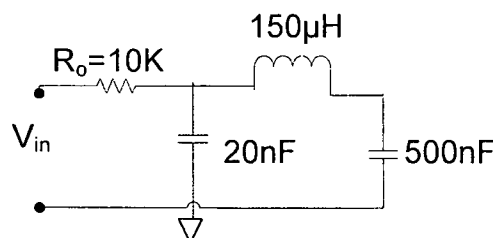


Figure-2

(OR)

- b)i) Draw Clapp oscillator using FET, Explain and derive the condition for oscillation (10)
- ii) In Colpitt's Oscillator $C_1=1\mu\text{F}$ and $C_2=0.2\mu\text{F}$. If the frequency of oscillation is 10KHz, find the value of inductor. Also find the required gain for sustained oscillation. (4)
- iii) Compare between Colpitt's and Clapp Oscillator. (2)

- 14)a) (i) Explain single tuned amplifier and derive for gain, resonant frequency and cutoff frequencies (10)
- (ii) A JFET tuned amplifier is tuned at 200 KHz using coil with $Q=100$ and $L=1.0\text{ mH}$, $g_m=2\text{mA/V}$ and $r_d=20\text{K}\Omega$. Find the values of loaded Q, tuning capacitance, bandwidth, maximum gain and gain at 5KHz of resonance. (6)

(OR)

- b) (i) List out the neutralization techniques that are used in the stability of tuned amplifiers. With the help of neat circuit diagram explain any one. (6)
- (ii) Explain the frequency response of a stagger tuned amplifier (6)
- (iii) Consider the design of an IF amplifier for FM radio receiver. Using two synchronously tuned stages with $f_o=10.7\text{ MHz}$ and 3-dB bandwidth of each stage so that the overall bandwidth is 200KHz. Using $3\text{-}\mu\text{H}$ inductors find C and R for each stage (4)

- 15))a) Explain the Buck-Boost Converter with the help of its relevant waveforms. Derive the equation for its output voltage, ripple current, critical values of inductance and capacitance. (16)

(OR)

- b)i) Explain Class-AB power amplifier utilizing the MOSFETs as output stage (10)
- (ii) In boost converter, $V_o=15\text{V}$, $V_{in}=5\text{V}$, $L=150\mu\text{H}$, $C=220\mu\text{F}$ and switching frequency=25 KHz. Calculate the values of Duty cycle, ripple current and ripple voltage. (4)
- (iii) Define Cross-over distortion. How to overcome it (2)