

Roll No.

--	--	--	--	--	--	--	--	--	--

B.E / B.Tech (Full Time) DEGREE ARREAR SEMESTER EXAMINATIONS, APRIL / MAY 2014
ELECTRICAL AND ELECTRONICS ENGINEERING
 Second Semester
EE 181/EE 9151-Electric Circuit Analysis
 (Regulations 2004/2008)

Time: 3 Hours

Answer ALL Questions

Max. Marks 100

PART-A (10 x 2 = 20 Marks)

1. Define lumped network.
2. Transform a voltage source of 20V with an internal resistance of 5Ω to a current source.
3. Draw the current response of RL series circuit excited from DC source.
4. Given $V(s) = \frac{s+2}{s(s+1)}$, determine the initial and final values of $v(t)$.
5. Two sinusoidal currents are given by $i_1 = 10 \sin(\omega t + \pi/3)$ and $i_2 = 15 \sin(\omega t + \pi/4)$. Calculate the phase difference show in phasor diagram.
6. Calculate the bandwidth between the half power points of circuit which resonant at 1MHz and has a Quality factor of 100.
7. Determine the maximum power transfer to the load is connected in series with $(15 + j20) \Omega$ and 50 Volts supply.
8. Mention the necessity of mesh impedance matrix with it application.
9. Find out the self-inductance of coil has 500 turns is linked with 50 mWb, when carrying a current of 125 A.
10. Give the relationship between line and phase voltages for star connected load with phasor diagram.

Part – B (5 x 16 = 80 marks)

11. (i) Determine the equivalent resistance between A and B in Fig.1a (8)
- (ii) Find the current through 1Ω resistor using Kirchoff's laws in Fig.1b. (8)

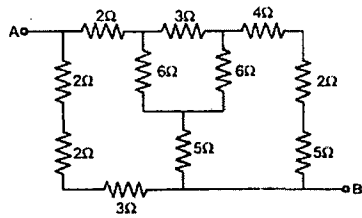


Fig.1a

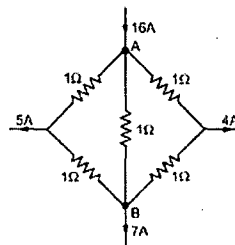


Fig.1b

12. a) A series RL circuit has $R=50 \Omega$ and $L=0.2 \text{ H}$ connected with $v(t) = 150 \sin(500t + \phi)$ volts is applied at $t=0$ when $\phi=0$. Find an expression for the value of current.

(OR)

- b) A series RLC circuit fed by a d.c. voltage of 50 V with $R=3000\ \Omega$, $L=10\ \text{H}$ and $C=200\ \mu\text{F}$ applied at $t=0$. Derive the expression for the current and its maximum value. Assume initial conditions to be zero.
13. a) A series RLC circuit with $R=100\ \Omega$, $L=0.5\ \text{H}$ and $C=40\ \mu\text{F}$. Determine the resonance frequency, lower and upper half power frequencies, Band width, quality factor, damping ratio and voltage across each element is 200V.

(OR)

- b) A series RL branch is connected in parallel with a pure capacitor C. Find the resonance frequency of combination if $R=250\ \Omega$ and $L=100\ \text{mH}$ and $C=0.005\ \mu\text{F}$. What is the value of dynamic resistance? If R, L and C are connected in series, calculate the new resonant frequency.
14. a) (i). Find the current through $3\ \Omega$ using Superposition theorem Fig.2a (8)
(ii) Find the current I in Fig.2b using Nodal analysis. (8)

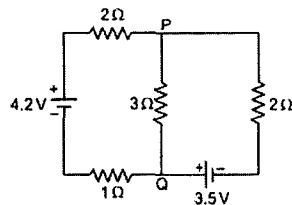


Fig. 2a.

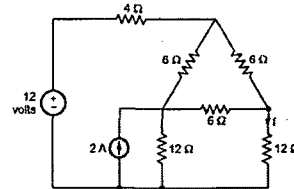


Fig. 2b.

(OR)

- b) (i). Find the current through $16\ \Omega$ using Thevenin's theorem in Fig.2c (8)
(ii) Determine the current through $3\ \Omega$ using Mesh analysis shown in Fig. 2d (8)

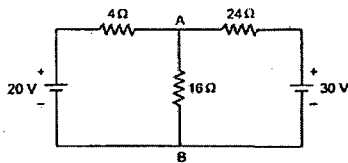


Fig. 2c.

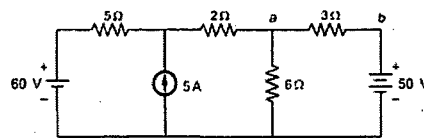


Fig. 2d

15. a) Two identical coils in series give an effective inductance of 800 mH and when one of the coils is reversed then the effective inductance of 400 mH. Determine self-inductances, mutual inductances between coils and the coefficient of coupling.

(OR)

- b) (i) The number of turns in two coupled coils are 600 and 1200 respectively. When a current of 4 A flows in coil 1, the total flux in coil 1 is 0.5 mWb and the flux linking coil 2 is 0.4 mWb. Determine the self-inductances of the coils and mutual inductance between them. Also calculate coefficient of coupling. (10)
- (ii) Two wattmeters are connected to measure the input of a 15 HP, 50 Hz, 3 ϕ at full load. The full load efficiency and p.f are 0.9 and 0.8 lagging respectively. Find the reading of the two wattmeters (6)