

B.E. (FULL-TIME) DEGREE END SEM EXAMINATIONS April/May 2012
 ELECTRICAL AND ELECTRONICS ENGINEERING
 III SEMESTER (REGULATION 2008)
 EE 9204: DIGITAL SYSTEM DESIGN

Time: 3 Hours

Max. Marks: 100

Answer ALL Questions

PART – A (10 x 2 = 20 Marks)


- 1 Express the Boolean function $F=xy+x'z$ in a product of maxterm form.
- 2 Design a combinational circuit with three inputs and one output. The output should be 1, when the binary value of the inputs is less than three. And 0 otherwise.
- 3 Construct a J K flip-flop using a D flip-flop.
- 4 What type of Register is needed to convert serial data to parallel and parallel data to serial
- 5 Write the differences between Synchronous and Asynchronous sequential Circuits
- 6
- 7 Describe the differences between a PLA and a PAL by using logic diagrams.
- 8 What is the noise margin for TTL? Explain its purpose
- 9 Draw a circuit to implement the following VHDL statement
 $A \leq B1$ when $C1 = '1'$ else $B2$ when $C2 = '1'$ else
 $B3$ when $C3 = '1'$ else '0' Where all the signals are of type bit.
- 10 Estimate how many AND gates and adders will be required for a 16-bit *16-bit array multiplier.

PART – B (5 x 16 = 80 Marks)

- 11 a (i) Given the Boolean function

$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$
 - Obtain the truth table of the function.
 - Draw the logic diagram using the original Boolean expression.
 - Simplify the function to a minimum number of literals using Boolean algebra.
 - Obtain the truth table of the function from the simplified expression
 - Draw the logic diagram from the simplified expression and compare the total number of gates.

 - 12 a (i) A sequential circuit has one flip-flop Q, two inputs x and y, and one output S. It consists of a full adder circuit connected to a D flip-flop as shown in the figure below. Derive the state table and state diagram of the sequential circuit.



OR

- b (i) A PN flip-flop has four operations: clear to 0, no-change, complement, and set to 1, when inputs P and N are 00, 01, 10 and 11 respectively.
- Tabulate the characteristic table
 - Derive the characteristic equation
 - Tabulate the excitation table
 - Show the PN flip-flop can be converted to a D flip-flop
- 13 a (i) Find the Critical race-free state assignment for the reduced flow table shown in the following figure

	00	01	11	10
a	a	d	a	c
b	a	b	b	d
c	d	c	b	c
d	d	d	e	d
e	f	c	e	c
f	f	b	a	f

OR

- b (i) An Asynchronous sequential circuit has two internal states and one output. The excitation and output functions describing the circuit are

$$Y_1 = x_1 x_2 + x_1 y_2' + x_2' y_1$$

$$Y_2 = x_2 + x_1 y_1' y_2 + x_1' y_1$$

$$Z = x_2 + y_1$$

- Draw the logic diagram of the circuit
- Derive the transition table and output map
- Obtain a flow table for the circuit
- Describe the behaviour of the circuit

- 14 a (i) Design a Synchronous sequential machine that will detect the input sequence 000, 010,101,001. When the correct sequence has been detected it causes an output Z_2 to go high. Any incorrect input sequence of four three-bit code words causes output Z_1 to go high. After an input sequence of four three-bit code words, cause the state machine to initialize in preparation of a new input.
- Determine the minimum EPROM size.
 - Identify inputs and outputs for the EPROM.
 - Construct the EPROM data table and
 - Draw the logic diagram including EPROM used and the state variable ICs used.

OR

- b (i) Sketch the circuit diagram for a TTL two input tri-state NAND gate. Identify the logic input and the control input. Explain the condition of each transistor in the circuit when the tri-state enable is active.
- (ii) Explain the purpose of Darlington pair found in the top transistor position of the TTL totem pole for the high speed and schottky subfamilies
- 15 a (i) Write a VHDL module that describes a 16-bit serial-in, serial-out shift register with inputs Serial input(SI), Enable(EN), and Clock shifts on rising edge(CK) and a Serial output(SO). [12marks]
- (ii) Write a VHDL Description of an S-R Latch using a process [4marks]
- OR
- b (i) Implement a 3-to-8 decoder using a LUT whose output should be an 8-bit unsigned vector. Give the LUT truth table and write the VHDL Code.
- (ii) Write VHDL code that finds the largest integer in the array of 20 integers.
- using a FOR loop
 - using a while loop