

3/10/13

5

BE (Regular) Degree End Semester Examinations, Nov/Dec 2013
II Semester
EC9152 Circuit Analysis
Reg-2009

Total Marks:100

PART-A (10 X 2 =20 Marks)

- 1) In a circuit $5\mu\text{J}$ of energy is required to transfer $0.1\mu\text{C}$ from point A to point B. Determine the electric potential difference that exists between the two points.
- 2) For the circuit in Figure-1, if $v_2=1000i_2$ and $i_2=5\text{mA}$, determine v_s .
- 3) Define super-position theorem.
- 4) Draw the dual of the circuit shown in Figure-2.
- 5) Find the angle by which i_1 lags v_1 if $v_1=120 \cos(120\pi t-40^\circ)$ and $i_1=-0.8\cos(120\pi t-110^\circ)$.
- 6) Find the average power being delivered to an impedance $Z_L=8-j11\Omega$ by a current $I=5\angle 20^\circ$.
- 7) At $\omega=1000$ rad/sec, Find a parallel network that is equivalent to series network shown in Figure-3.
- 8) The Circuit shown in Figure-4 has been in the form shown for very long time. The switch opens at $t=0$. Find i_R at t equals to ∞ .
- 9) A $480/2400$ Vrms step-up ideal transformer delivers 50KW to a resistive load. Calculate the turns ratio.
- 10) Two coils with inductances in the ratio of four to one have a coupling coefficient $k=0.6$. When these coils are connected in series aiding, the equivalent inductance is 44.4mH . Find L_1 , L_2 and M .

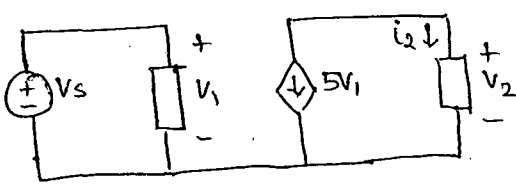


Figure-1

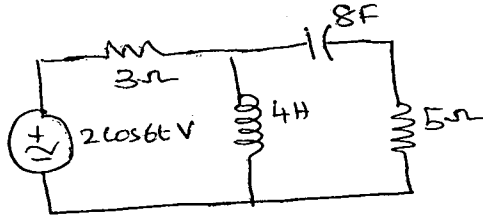


Figure-2

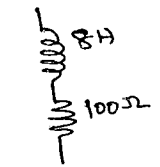


Figure-3

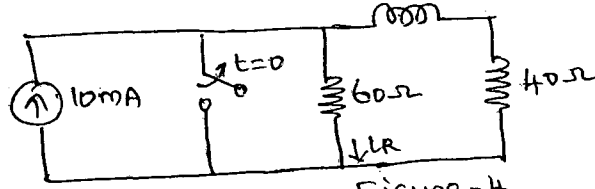


Figure-4

PART-B (5 X 16 =80 Marks)

- 11) i) For the circuit of Figure-5, find the currents $i_1(t)$, $i_2(t)$ and $i_3(t)$ if $f=50\text{Hz}$. (8)
- ii) Find the value of v_x and v_y in the circuit of Figure-6. (8)

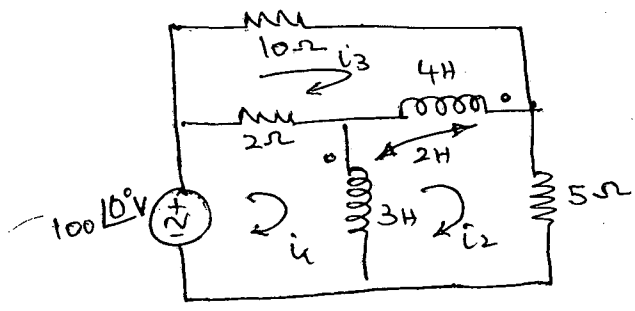


Figure-5

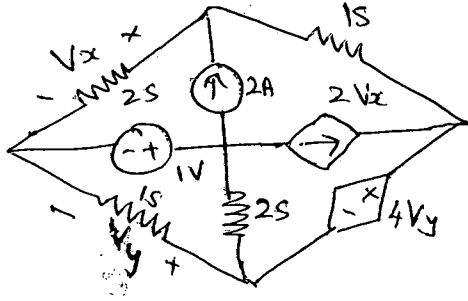


Figure-6

- 12)a)i) Find V_1 in the circuit of Figure-7 using source transformation. (6)
 ii) Determine the Thevenin and Norton equivalents of the network shown in Figure-8. (10)

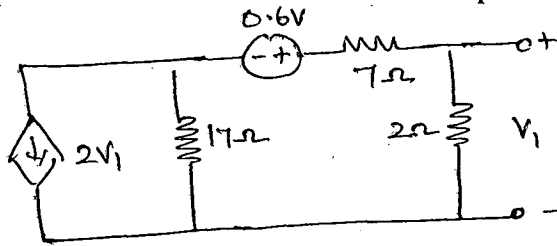


Figure-7

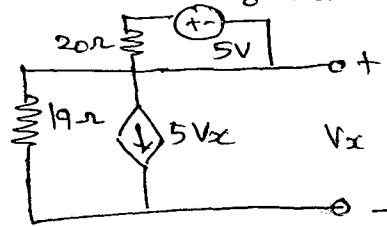


Figure-8

(OR)

- b)i) The circuit shown in Figure-9 depicts a circuit separated into two stages. Select R_1 , so that maximum power is transferred from stage 1 to stage 2. (8)
 ii) Replace the network in Figure-10 with an equivalent three- Δ network. (8)


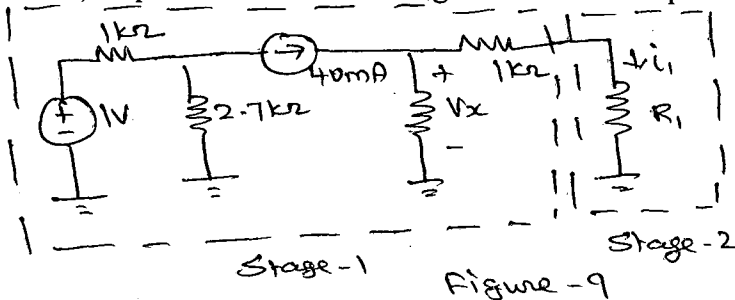


Figure-9

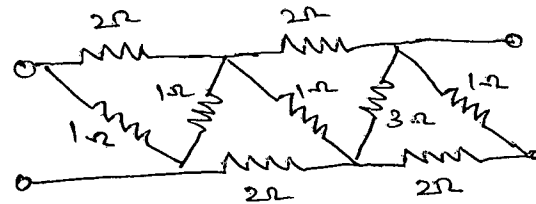

- 13)a)i) In the circuit shown in Figure-11, calculate the average power generated by each source and the average power delivered to each impedance. (8)
 ii) Two admittances, $Y_1=3+j4$ mS and $Y_2=5+j2$ mS, are in parallel, and a third admittance, $Y_3=2-j4$ mS is in series with the parallel combination, If a current $I_1=0.1\angle 30^\circ$ A is flowing through Y_1 , find the magnitude of the voltage across (a) Y_1 , (b) Y_2 , (c) Y_3 (d) the entire network. (8)

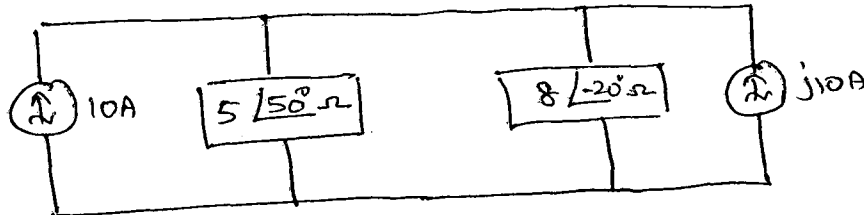


Figure-11

(OR)

- b) Use superposition to find $v_1(t)$ and $v_2(t)$ in the circuit of Figure-12. (16)

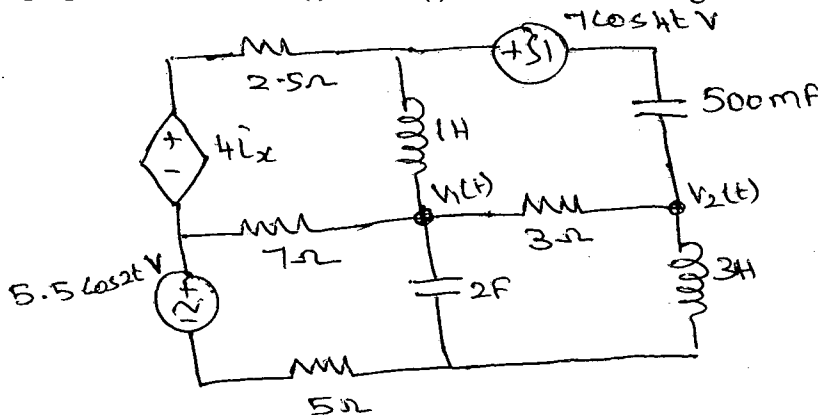


Figure-12

- 14)a)i) For the circuit in Figure-13, find i_x , i_y and power absorbed by 3Ω resistor. (8)
 ii) For the circuit of Figure-14, compute the voltage across each current source. (8)


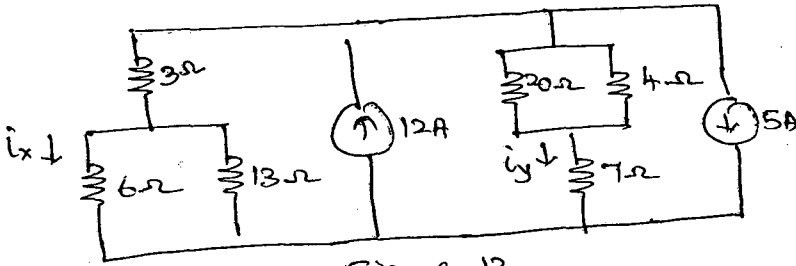


Figure-13

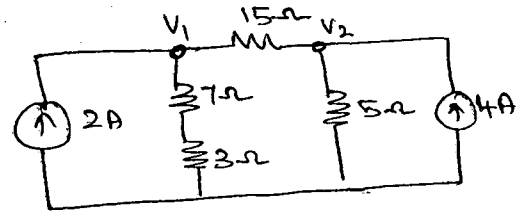

(OR)

- b)i) Determine the current i_1 in the circuit of Figure-15. (8)
 ii) Use Ohm's and Kirchhoff's law on the circuit of Figure-16, to find (a) v_x , (b) i_1 (c) I_s and (d) power provided by the dependent source. (8)

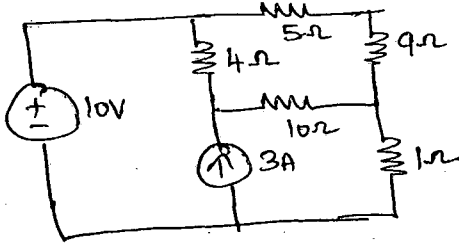


Figure-15

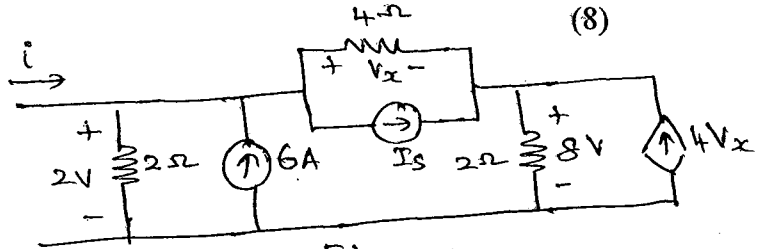


Figure-16

- 15)a)i) For the circuit of Figure-17, find $v_c(t)$ at t equal to (a) 0^- (b) 0^+ (c) ∞ (d) $0.08s$. (8)
 ii) A series resonant network consists of a 50Ω resistor, a $4mH$ inductor, and a $0.1\mu F$ capacitor. Calculate values for (a) ω_0 (b) f_0 (c) bandwidth (d) Q -factor. (8)

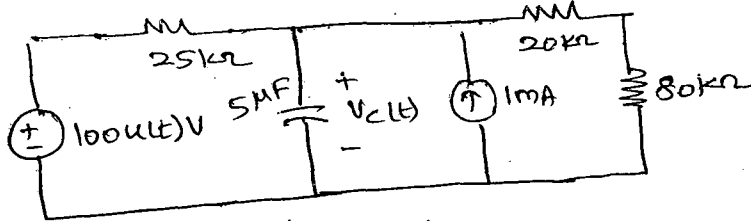


Figure-17

(OR)

- b)i) The switch of Figure-18 has been open for a long time before it closes at $t=0$. For the time interval $-5 < t < 5\mu s$ sketch (a) $i_L(t)$ (b) $i_x(t)$. (8)
 ii) The switch in the circuit shown in Figure-19 has been closed for a very long time. It opens at $t=0$. Find $v_c(t)$ for $t > 0$. (8)

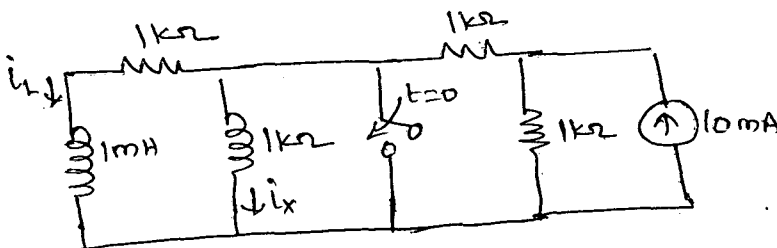


Figure-18

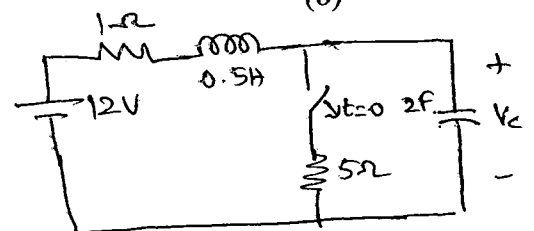


Figure-19