

25/4/13

Roll No.									
----------	--	--	--	--	--	--	--	--	--

B.E./B.Tech. (Full Time) DEGREE END SEMESTER EXAMINATIONS, APRIL/MAY 2013  
 ELECTRONICS AND COMMUNICATION ENGINEERING BRANCH  
 FOURTH SEMESTER

17

**EC 281 – DIGITAL ELECTRONICS AND SYSTEM DESIGN**  
 (REGULATIONS 2004)

Duration: 3 Hours

Max.marks: 100

Answer ALL questions

**PART-A**

**(10x2=20 Marks)**

1. Write an example for self-complementary code.
2. What is meant by weighted code?
3. Define noise margin.
4. What is meant by Fan out?
5. Realise full adder using appropriate decoder.
6. Implement  $f(x,y,z)=(0,2,6,7)$  using multiplexer.
7. What is asynchronous sequential circuit?
8. Derive the characteristic equation of SR flip flop.
9. What is fundamental mode machine?
10. Define static -0 and static -1 hazard.

**PART-B**

**(5x16=80 Marks)**

11. Design a code converter to convert 4-bit Gray to Binary. (16)
- 12.(a) Draw the circuit of basic open collector TTL gate and explain its functions. (16)
- OR
- 12.(b) Draw the circuit of CMOS inverter gate and explain its function. Write the merits and demerits of CMOS family. (16)
- 13.(a) Design a BCD adder and draw the logic diagram. (16)
- OR
- 13.(b)(i) Design a full subtractor with suitable multiplexers and draw the logic diagram. (8)
- (ii) Write a short note on priority encoder. (8)
- 14.(a) Design a synchronous sequential circuit counting in the following sequence 0,1,3,7,6,4, and repeat. Use JK flipflop. (16)
- OR
- 14.(b)(i) Draw the logic diagram of bidirectional shift register and explain its functions. (8)
- (ii) Design a Johnson counter for generating 10 timing signals. (8)
- 15.(a) Explain the cycles and races with suitable examples. (16)
- OR
- 15.(b) Explain about essential hazards and pulse mode circuits. (16)

-----