

15/11/13

--	--	--	--	--	--	--	--

25

B.E Full Time Degree END SEMESTER EXAMINATIONS, Nov/Dec 2013

Fifth Semester, EEE / R- 2008

EE 9303 Linear Integrated Circuits

Time: 3 Hours

Max. Marks: 100

Answer ALL Questions

PART – A (10 x 2 = 20 Marks)

1. How are Integrated Circuits categorized?
2. List the ideal characteristics of OpAmp.
3. If in a OpAmp IC ,a 0.3 mV change in common mode input causes a DC output offset change of 3mV,determine the CMRR in dB.
4. Write briefly on the R-2R ladder type D/A converter.
5. What is the need for converting a First order Filter into a Second order filter?
6. Discuss on a suitable circuit suited to detect the aperiodic sinusoidal input waveform using OpAmp.
7. If V (DC) is 15V, v(ripple: peak to peak) is .25v determine the ripple factor & the percentage ripple.
8. What is meant by Lock range in a PLL circuit?
9. What is the need for optocoupler ICs?
10. Distinguish the principle of Linear regulator and a switched mode power supply.

PART – B (5 x 16 = 80 Marks)

11.
 - i) Derive the functional parameters for an Inverting mode feedback circuit with OpAmp.
 - ii) For a 741 OpAmp IC Inverting mode ,with $R_1=1\text{Kohm}$, $R_f=4.7\text{ Kohm}$, compute A_f ; R_{if} ; R_{of} ; BW; offset voltage.
 - (iii) Develop a Comparator Logic of the circuit by finding for $(A>B)$; $(A=B)$ using differential mode OpAmp and suitable components if required. (6+6+4)
12.
 - a.
 - i. What are the advantages of integrating type A/D converters?
 - ii. Design a OpAmp based Integrator circuit.
 - iii. Discuss on the Integrating type ADC realization using OpAmp. (2 + 7+7)

(OR)

12. b. i). What are the types of voltage comparator techniques?

....2

- 2 -

- ii) For an open loop inverting mode OpAmp, if v_{in} = 2V peak to peak sine wave at 500Hz, supply voltages=15V DC fitted with external pot that changes the $V(Ref)$ =0V; 0.2V; - .5V. Draw the output waveforms.

- iii) Design & explain a Schmitt Trigger circuit. (2 + 7+7)

13. a Design a Sine wave Generator using OpAmp to output a frequency of 1.5 KHz , with $C = .01 \mu F$. What is the design attribute in the circuit to obtain a cosine wave generation? (10 + 6)

(OR)

13. b. Write briefly on any two of the following: (8 + 8)
- Successive Approximation Type A/D converter.
 - Diodes role in OpAmp Circuits.
 - Clipper and Clamper circuits.

14. a. i) How are Filters categorized?
ii) Design a Analog First order Low pass Filter using OpAmp.
iii) How is the Low Pass filter converted to High pass filter of First order?

(2+10+4)

(OR)

14. b. Design a Square Wave Generator. Explain how a Triangular Wave ; Sawtooth wave is Generated with this circuit. (8+4+4)

15. a. (i) Describe the 555 Timer IC .(ii)Design a Astable Multivibrator Circuit to generate output Pulses of 25%,50% duty cycle using a 555 Timer IC, with choice of $C=0.05\mu F$, Frequency as 2.0KHz . (8+8)

(OR)

15. b. Answer any two of the following: (8+8)
- Switched capacitor filters.
 - LM 380 power amplifier.
 - IC Fabrication technique to realize diode, Transistor.