

**B.E DEGREE EXAMINATIONS APRIL/MAY 2012**  
**DEPARTMENT OF ELECTRONICS AND COMMUNICATIONS**  
**FOURTH SEMESTER FULL TIME (R 2008)**  
**EC9252 ELECTRONIC CIRCUITS II**

TIME:3hrs

MAX MARKS:100

INSTRUCTIONS:ANSWER ALL QUESTIONS

PART A


(10x2=20marks)

1. Derive for series and parallel resonant frequencies of a crystal using its equivalent circuit
2. Draw the equivalent circuit of a transconductance amplifier
3. For an ac Voltage controller with  $Z_L = R + jX_L$ , draw the controlled ac current waveform with respect to ac input for two cycles, showing clearly the firing and extinction angles.
4. Derive the ripple factor for a FWR with L filter.
5. A BJT RC Phase shift oscillator has  $f_o = 10$  KHz,  $R_{IN} = 6.8K$  and  $R_O = 8K$ , calculate the Voltage gain and current gain of the amplifier at  $f_o$ .
6. Calculate the minimum time interval between consecutive triggers for an BJT Mono stable multivibrator with  $V_{CC} = 20v$ ,  $R_C = 9.8k$ ,  $R_B = 930k$ ,  $R_1 = 860k$ ,  $R_2 = 65k$  and  $C = 0.1\mu F$ .
7. A single tuned amplifier is designed to receive voice signal over AM broadcast at 1550KHz. What is the quality factor.
8. Draw and specify the features of any one configuration of tuned amplifier with multiple tuned Circuits used in video amplifier IC.
9. Justify that current shunt feedback increases the output impedance with topological diagram
10. A simple RC Circuit produces a sweep voltage of two volts from 15v supply Find all three linearity errors.

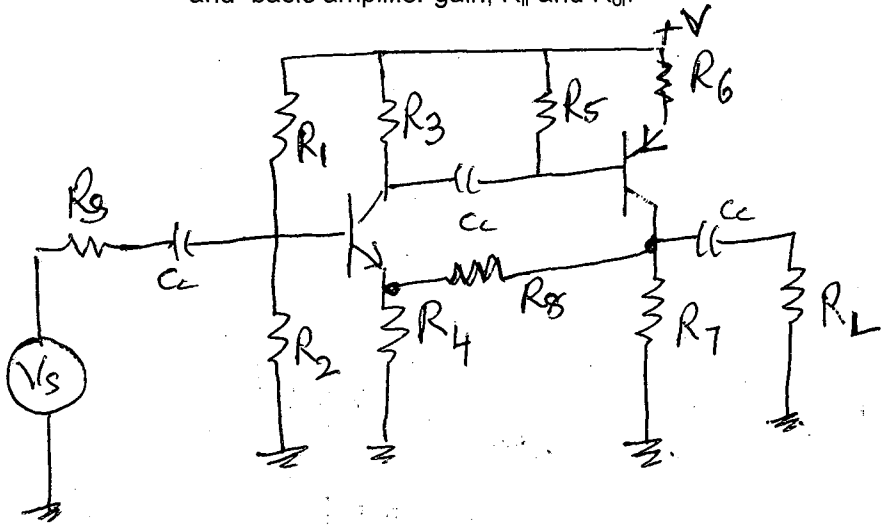PART B

(16x5=80 marks)

- 11(i) A single stage transresistance amplifier having 82KHz bandwidth and  $R_C = 5K$  is given negative feedback of .02mA/v so as to increase the bandwidth to 410 KHZ. Draw the transresistance amplifier with and without feedback. Calculate  $A_{Vf}$ ,  $A_{if}$ ,  $R_{mf}$  and  $G_{mf}$  using negative feedback concept [Assume  $h_{fe} = 183$  and  $h_{ie} = 3.2k$ ] (8)
- (ii) Draw the basic amplifier of the feedback amplifier shown below. With the equivalent circuit derive expressions for feedback factor and basic amplifier gain,  $R_{if}$  and  $R_{of}$ . (8)



- 12a (i) Derive and explain the transfer function of a wein network and draw the bode plots. (6)  
(ii) Construct an oscillator circuit using the above network and explain its working, also derive for its frequency of oscillation (10)

OR

- b. With Circuit diagram of clapp oscillator and its equivalent circuit derive for its frequency of oscillation and design considerations to be met to get sustained oscillation

- 13a. (i) Explain with circuit diagram a Boost Converter and derive for  $V_o$  and Critical values of inductance and capacitance. (10)  
(ii) A Boost Converter has an input voltage of 6V The average load current is 0.5A, the switching frequency is 25KHz,  $L = 150 \mu H$  and  $C = 220 \mu F$ , calculate duty cycle, ripple current of inductor and critical values of inductor and capacitor (6)

OR

- b. (i) Describe how output Voltage is regulated with respect to line and load variations using linear Voltage Regulator (10)  
(ii) With structural diagram and equivalent circuit of IGBT, explain the V-I Characteristics of IGBT. (6)

- 14a. (i) Draw emitter coupled Bistable multivibrator and explain its hysteresis Characteristics. (8)  
(ii) Design a BJT free running, Collector coupled multivibrator to generate a pulse waveform of (0 – 10V) with 70% duty cycle at 2KHz. Draw the waveforms at base and Collector terminals of both the active devices. (8)

OR

- b. (i) Explain current sweep generator (12)  
(ii) Describe the design aspects of speed up capacitor (4)

- 15a. (i) Draw a single tuned amplifier and with its equivalent circuit, derive for  $A(f)$  and cut-off frequencies (10)

- (ii) A cascaded Synchronous tuned amplifier is designed to receive a signal centered at 10.7MHz having bandwidth of 400 KHz, using single tuned amplifiers with  $L = 3 \mu H$  and  $Q_L = 13.61$  Draw the designed circuit and its frequency response [Assume relevant data] (6)

OR

- b. (i) Design a tuned amplifier shown with amplifier shown with  $L = 5 \mu H$ ,  $R_p = 1K$  to receive 455 KHz. Find its bandwidth, tuning capacitor  $C_1$  and current gain  $I_o/I_1$  if  $R_{in} = 1K$  and  $C_{in} = 200$  pf (without tapping of coil) (10)  
(ii) Adjust the tapping ratio of the coil of the circuit shown to reduce the BW to 10 KHz Also find the new value of  $C_1$  and current gain at resonance. (6)

