

REG:NO:

9

**B.E./ B.Tech (Full Time) DEGREE END SEMESTER EXAMINATION, APRIL / MAY 2012**

**ELECTRONICS AND COMMUNICATION ENGINEERING**

**FOURTH SEMESTER**

**EC283 – LINEAR INTEGRATED CIRCUITS**

**(REGULATIONS 2004)**

**Time: Three hours.**

**Maximum: 100 marks**

**Answer All Questions.**

**Part A**

**10 X 2 = 20 Marks.**

1. Draw the pin detail of IC 741.
2. Give the schematic of Wilson current source?
3. Draw the schematic of zero crossing detector using op-amp.
4. What is a logarithmic amplifier?
5. What is an analog multiplier?
6. Define PLL.
7. What is a data converter?
8. Give the schematic of sample and hold circuit.
9. List different sources of noise.
10. Draw the schematic of power amplifier.

**Part B**

**5 X 16 = 80 Marks.**

- 11(a)(i). With a neat block diagram and schematic explain the internals of op-amp. (8)
- (ii). Briefly explain the method of improving slew rate. (8)
- 12.(a)(i). With a neat diagram explain non inverting amplifier and derive its output equation. (8)
- (ii). Briefly explain the construction of op amp based window detector. (8)

**(OR)**

**P.T.O**

12.(b).With a neat diagram and derivation explain the working of 3 op-amp based instrumentation amplifier. (16)

13.(a). With a neat diagram explain the working of voltage controlled oscillator. (16)

**(OR)**

13.(b).(i). Explain the construction of AM modulator using PLL. (8)

(ii). Write short notes on frequency synthesizers. (8)

14.(a).(i). With a neat diagram explain the working of high speed sample and hold circuits. (8)

(ii). Briefly explain the construction of voltage to frequency converter (8)

**(OR)**

14.(b).(i).Explain the working of R-2R ladder type DAC. (8)

(ii).Explain the working of single slope ADC. (8)

15.(a).With a neat diagram explain the working of 555 timer IC. Design a circuit using the same IC to toggle an LED with one second delay assume all other relevant details. (16)

**(OR)**

15.(b).(i).Using the power amplifier circuit design an intercom, assume all other relevant details. (8)

(ii). Write short notes on voltage regulators. (8)

---