

13.5.19

Roll No.

--	--	--	--	--	--	--	--	--	--

B.E (FT) END SEMESTER EXAMINATIONS – APRIL / MAY 2019
ELECTRONICS AND COMMUNICATION ENGINEERING
(Common to Bio-Medical Engineering)
4th Semester

EC8452 OPERATIONAL AMPLIFIERS AND ANALOG INTEGRATED CIRCUITS

Time: 3 Hours (Regulation 2012) Answer ALL Questions Max. Marks 100

PART-A (10 x 2 = 20 Marks)

1. An non-inverting amplifier with a gain of 100 is nulled at 25°C. What will happen to the output voltage if the temperature rises to 50°C for an offset voltage drift of 0.15mV/°C?
2. Find the maximum frequency for a sine wave output voltage of 10V peak with an OPAMP whose slew rate is 1V/μs.
3. Design a Schmitt trigger circuit with the following parameters: UTP = LTP = 1V, V_{cc} = ±15V.
4. What is meant by a “precision diode” and mention its application?
5. Draw the pin configuration of IC 565.
6. Define voltage to frequency conversion factor.
7. Draw the circuit diagram of a S/H circuit
8. A basic step of a 9-bit DAC is 10.3mV. If 000000000 represents 0V, what output is produced if the input is 101101111?
9. Mention the different types of noise.
10. State the limitations of a two terminal regulator IC.

PART-B (5 x 16 = 80 Marks)

- 11.(i) With neat diagram, derive the expression for Widlar Current source and also design a Widlar current source for generating a constant current I₀ = 10μA. Assume V_{cc} = 10V and V_{BE} = 0.7V, β = 125, V_T = 25mV. (10)
 - (ii) Discuss in detail about the stability of an OPAMP. (6)
 - 12.a)(i) Derive the output expression of the instrumentation amplifier with three OPAMPS. (10)
 - (ii) Draw an OPAMP circuit whose output is 5V₁ + 2V₂ - 5V₃ - 2V₄. (6)
 - (OR)
 - 12.b)(i) Derive and design a first order low pass filter with the frequency of 2KHz. Assume C = 0.1μF and the gain A = 2. (10)
 - (ii) For a non-inverting amplifier, R₁ = 1KΩ and R_f = 10KΩ, calculate the maximum output offset voltage due to V_{os} and I_B. The OPAMP is LM307 with V_{os} = 10mV and I_B = 300nA, I_{os} = 50nA. Calculate the value of R_{comp} to reduce the effect of I_B. Calculate the maximum output offset voltage with R_{comp}. (6)
- (P.T.O)

13/5/19
(AN)



- 13.a)(i) Construct the four quadrant transconductance multiplier and derive its output expression. (10)
(ii) With a neat diagram, explain how a frequency synthesizer circuit using PLL IC 565. (6)
(OR)
- 13.b)(i) Explain the operation of VCO with neat block diagram and derive its frequency of oscillation. (10)
(ii) Calculate the output frequency f_o , lock range Δf_L and capture range Δf_c of a 565 PLL if $R_T = 6.8k\Omega$, $C_T = 0.001\mu F$ and $C = 1\mu F$. (6)
- 14.a)(i) A 8-bit A/D converter accepts an input voltage signal of range 0V to 9V. What is the minimum value of the input voltage required for generating a change of one least significant bit?. Specify the digital output for an input voltage of 4V. What input voltage will generate all 1s at the A/D converter output? (8)
(ii) Explain in detail about the operational features of 4-bit weighted resistor type D/A converter. (8)
(OR)
- 14.b)(i) With neat diagram and necessary waveforms, explain the working of voltage to time converter. (8)
(ii) Briefly explain the operation of digital switches used for DAC. (8)
- 15.a)(i) Briefly explain the working principle and functionalities of LM 380 audio amplifier. (10)
(ii) Describe in detail the working of an optocoupler. (6)
(OR)
- 15.b) With neat functional diagram, explain the working of 555 timer as monostable multivibrator and also derive an expression for the frequency of oscillation with relevant waveforms. (16)
-

