

Roll No.

--	--	--	--	--	--	--	--	--	--

B.E ( Full Time ) DEGREE END SEMESTER EXAMINATIONS, APRIL/MAY 2019

ELECTRICAL & ELECTRONICS ENGINEERING

EE 8301 Digital Systems  
(Third semester)

(Regulation 2012)

Time: 3 hours *Past-A* (10 x 2 = 20) Answer ALL Questions Max Marks: 100

- Determine the base 'b' in each of the following cases : (i)  $(361)_{10} = (551)_b$  (ii)  $(859)_{10} = (5B7)_b$
- Write the 8-bit signed magnitude, 2's complement and 1's complement form of the decimal number (-13)
- Using the theorems of Boolean algebra simplify the following Boolean expression.  $f_1(A,B,C,D) = B + BCD + B'CD + AB + A'B + B'C$
- Express the three-variable function  $f(A,B,C) = \sum m(0,1)$  as a product of max terms
- A combinational circuit is described by the equations  $f_1(A,B,C) = ABC + A'B'C$   $f_2(A,B,C) = A'B'C' + A'BC$  ; Design a circuit which will implement these two equations using a decoder with an AND gate external to the decoder.
- Implement the following four variable Boolean function using four input multiplexers and NAND gates.  $f(A,B,C,D) = \sum m(0,7,8,9,10,11,15)$  Use B and C as control variables.
- Give the truth table and excitation table of SR Flip Flop.
- Draw the circuit diagram of three bit up-counting-ripple counter
- Differentiate asynchronous and synchronous circuits.
- Differentiate combinational logic and sequential logic circuits.

Part-B

5 x 16 = 80

- (i) Design a three bit synchronous counter that goes through the following states 1,2,4,6,0... use T FFs for realisation. (12)
- (ii) Design a four bit binary down counter(ripple) (4)

12.(a)(i) Design a full adder circuit. (8)

(ii) Reduce the Boolean function  $f(A,B,C,D) = \sum (0,1,2,3,4,8,10,12,14)$  using Karnaugh map and implement using gates. (8)

(OR)

12(b) Design a BCD to 2421 code converter using AND, OR and Invert gates.

13(a) (i) Implement the following 4-variable functions using 3 x 8 decoders having active low outputs and NAND gates:

$$f_1 = \sum m(0, 1, 3, 9, 12, 14)$$

$$f_2 = \sum m(5, 9, 12, 13, 15)$$

$$f_3 = \prod M(0, 3, 8, 11, 12, 15)$$

$$f_4 = \prod M(1, 2, 7, 8, 11, 12, 14)$$

(8)

(ii) Construct a 5X32 decoder with four 3 x 8 decoders with enable inputs and one 2 x 4 decoder. (4)

(iii) Draw the internal circuit diagram of a 8 x 1 multiplexer and give the truth table. (8)

(OR)

13(b)(i) Implement the following 4-variable Boolean function using 4-input multiplexers and NAND gates:  $f(A,B,C,D) = \sum m(0, 1, 3, 5, 6, 8, 9, 11, 12, 13)$  control variables A and B (6)



- (ii) Give a brief description about PAL (4)
- (iii) Implement the following 4-variable functions using a 16 x 4 ROM:
- $$f_1 = \sum m(0, 1, 3, 9, 12, 14)$$
- $$f_2 = \sum m(5, 9, 10, 12, 13, 15)$$
- $$f_3 = \sum m(0, 3, 8, 11, 12, 15)$$
- $$f_4 = \sum m(1, 2, 7, 8, 11, 12, 14)$$
- (6)

14 (a) For the sequential network shown in figure-1, (16)  
 derive the state table and draw the state diagram. What is the function of the circuit?


 


Figure 1

 

(OR)

14.b) Design a synchronous counter that goes through the sequence ...2,3,7,9,10,12,2....  
 Use JK FFs for implementation. (16)

15(a) Design a synchronous modulo-11 counter using NAND gates and T flip-flops  
 (OR)

15(b) Analyse the circuit shown in Figure-2

- (i) Determine the state table.
- (ii) Determine the state diagram.
- (iii) Use the state table to determine the output response to the input sequence  $X_1X_2 = 00, 01, 11, 10, 00, 01, 11, 01, 11, 10, 00$ .  
 Assume the initial conditions are  $X_1 = X_2 = 0$  and  $A = B = 0$ .

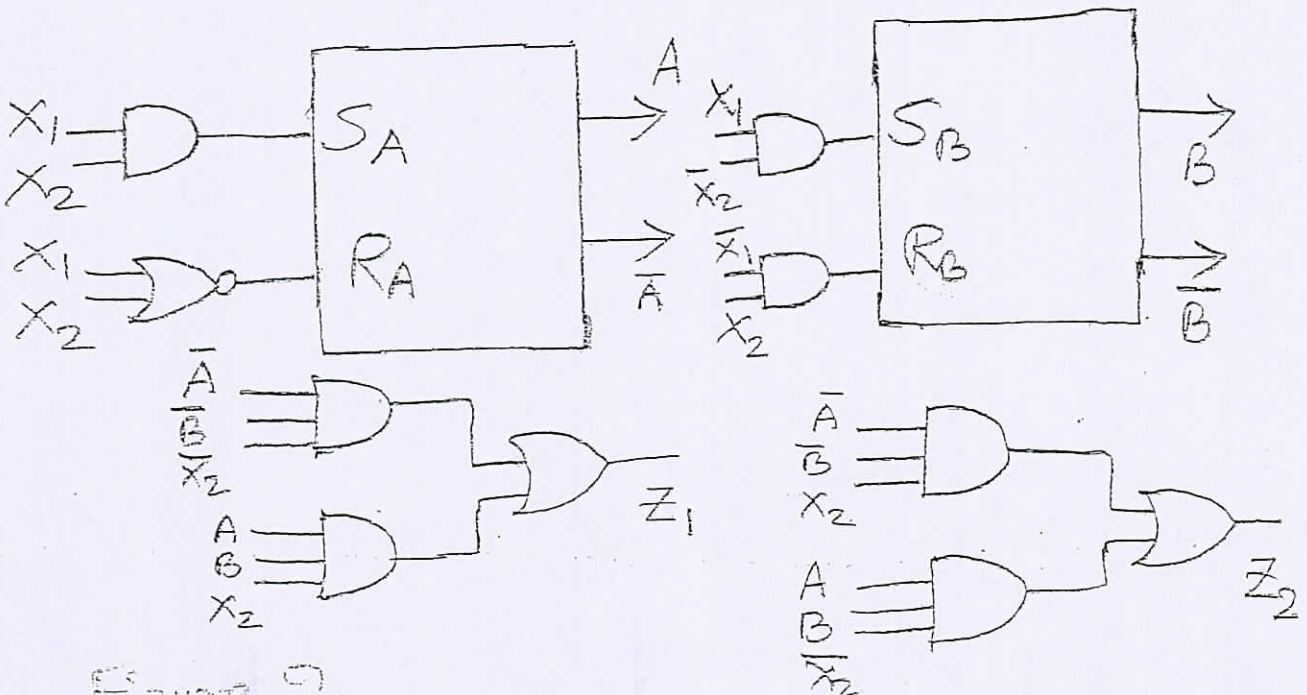


Figure 2