









	receiver. Explain one main advantage and one main disadvantage of each. In your block diagrams, normally which individual block is expected to have the best Noise Figure and which one block is expected to have the best IIP3.	+2		
(ii)	An Engineer is to design a receiver for space applications with no concern for interferers. The engineer constructs the heterodyne front end as shown in the block diagram given in Fig.7, avoiding band select and image select filters. Explain with the help of spectrum why this design suffers from a relatively high noise figure.	3		
12 (a) (i)	Consider the resistor terminated amplifier diagram shown in Fig.8. Here, 'A' represents the voltage gain of the amplifier, and $V_n$ represents the equivalent input noise of the amplifier. $V_{in}$ represents the input signal source. Assume that the internal amplifier block shown as triangle has infinite input impedance. Compute the total meansquare noise voltage at the output. In order determine the NF of the system, compute the meansquare noise voltage at the output assuming only the $R_{s1}$ associated in $V_{in}$ contributes noise (source contribution alone at the output). Based on these, write down the expression for the Noise Figure.	10	CO2	L3
(ii)	The circuit shown in Fig.9a is a fully differential version of the resistively terminated and its symmetric half equivalent circuit is also shown in Fig.9b. Using the steps outlined part (i) above, determine the expression for the overall Noise Figure of the fully differential system.	3		
<b>OR</b>				
12 (b) (i)	Assuming the input output relationship of an amplifier is given by $v_o(t) = c_0 + c_1 v_i(t) + c_2 (v_i(t))^2 + c_3 (v_i(t))^3$ , determine the expressions for IIP3 and input P1dB of this system.	10	CO2	L3
(ii)	An amplifier has a small signal gain of 12dB and OIP3 of 13dBm. What is the IM3 at an input of -10dBm.	3		
13 (a)	Derive the frequency of oscillations for the Colpitts oscillator shown in Fig.10 and indicate the assumptions/approximations you need to make use of. Also sketch the expected drain current waveforms of M1 and give the possible expression for the possible amplitude of $V_{out}$ .	8+5	CO2	L2
<b>OR</b>				
13 (b) (i)	Draw the circuit diagram of a Gilbert cell mixer and determine the expression for its conversion gain.	7	CO2	L2
(ii)	Indicate all the sources of Noise in the above Gilbert cell. Explain which transistors of the Gilbert cell contribute to the nonlinearity of mixer and which ones contribute 1/f noise at the output.	6		
14 (a) (i)	Explain why a charge pump used along with the phase detector? Justify this with its phase response and transfer function.	7		L4
(ii)	Explain how an analog multiplier can be used as a phase detector. Sketch its transfer characteristic and give the expression for its $K_{PD}$ .	6	CO3	
<b>OR</b>				
14 (b)	The block diagram in Fig.11 represents the phase transformations from the input to the output of a certain synthesizer. Write down the expression for the phase transfer function and explain why this block diagram and associated synthesizer would not be of use unless it is modified. With justification, suggest any suitable modification to this block diagram to make the synthesizer work. Assuming the input reference frequency for such a PLL is $f_{ref}$ , what is the minimum frequency step size one can get for the output of the synthesizer.	5+6 +2	CO3	L4
15 (a)	Consider the amplifier shown in Fig.12 for which the input to the gate terminals of M1 and M2 are as shown. $V_{th}$ represents the threshold	13	CO2	L3

	voltage of the M1 and M2. With justification, state what class of power amplifier this circuit represents. Sketch the possible drain current waveforms of M1 and M2 and also waveform of the current through RL. Explain atleast two functions/tasks carried out by the transformer.			
OR				
15 (b)	Draw the circuit diagrams of a differential LC oscillator and a ring oscillator. Explain the conditions necessary for establishing oscillations in each of these and give the expression for the frequency of oscillations.	3+3 +3+ 4	CO2	L3

**PART- C (1 x 15 = 15 Marks)**  
(Q.No.16 is compulsory)

Q. No	Questions	Marks	CO	BL									
16. (i)	Consider two amplifiers A and B with the noise characteristics given below. <table border="1" style="margin: 10px auto;"> <thead> <tr> <th></th> <th><math>(I_n)</math> (fA/√Hz)</th> <th><math>(V_n)</math> (nV/√Hz)</th> </tr> </thead> <tbody> <tr> <td>Amp A</td> <td>50</td> <td>10</td> </tr> <tr> <td>Amp B</td> <td>25</td> <td>20</td> </tr> </tbody> </table> <p>What is the optimum source resistance for each case. If the source resistance of 100K ohms, which amplifier is better. What is the minimum noise figure in each case.</p>		$(I_n)$ (fA/√Hz)	$(V_n)$ (nV/√Hz)	Amp A	50	10	Amp B	25	20	2+2+2	CO3	L5
	$(I_n)$ (fA/√Hz)	$(V_n)$ (nV/√Hz)											
Amp A	50	10											
Amp B	25	20											
16. (ii)	It is desired to downconvert the spectrum shown in Fig.13 using the different ideal LO frequencies. The figure shows the LO spectrum for $\omega_{LO} < \omega_1$ . (i) Sketch the downconverted spectrum for this case $\omega_{LO} < \omega_1$ , (ii) for the case when $\omega_1 < \omega_{LO} < \omega_2$ and also (iii) for the case when $\omega_2 < \omega_{LO}$ .	4											
16. (iii)	A load impedance of $R_L = 50$ ohms is to be matched to a source impedance of $R_s = 50$ ohms. The centre frequency is 1GHz. Design a suitable impedance matching network.	5											

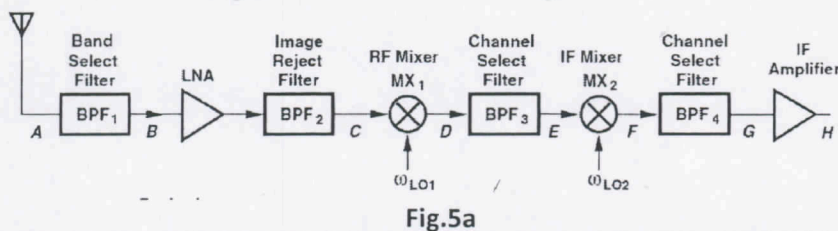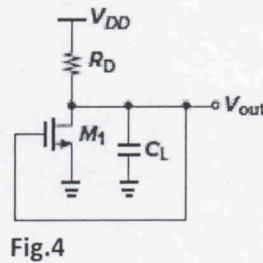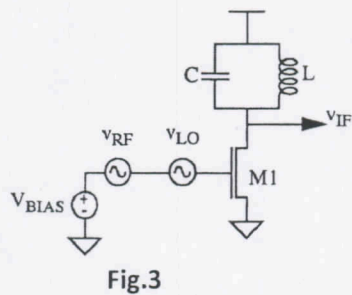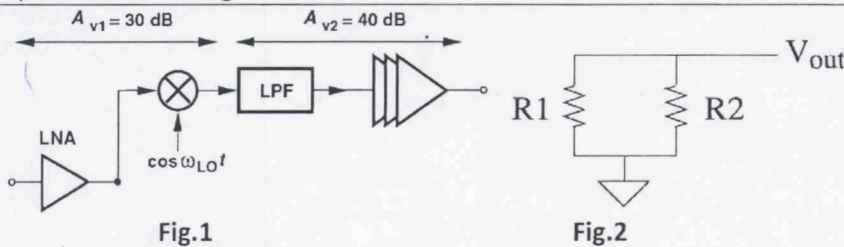

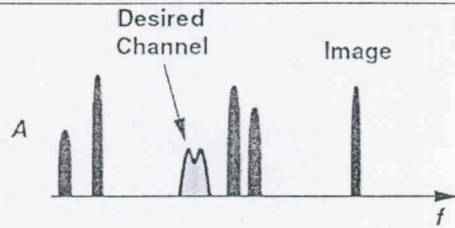


Fig.5b

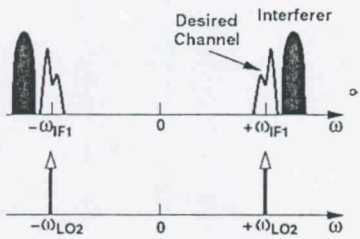


Fig6

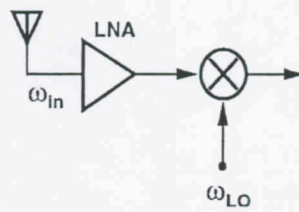


Fig.7

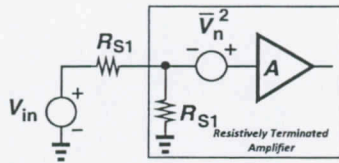


Fig.8

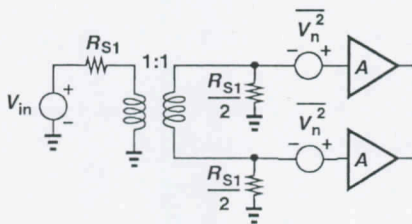


Fig.9a

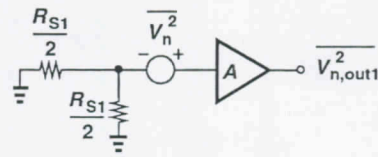


Fig.9b

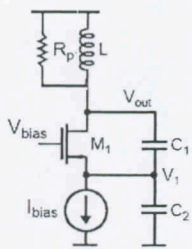


Fig.10

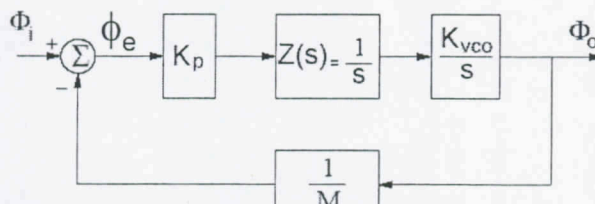


Fig.11

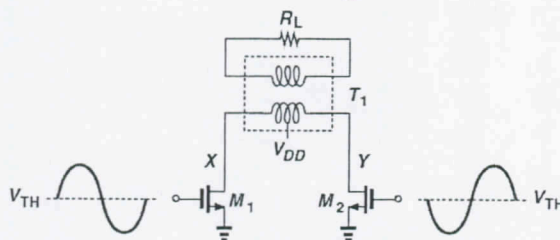


Fig.12

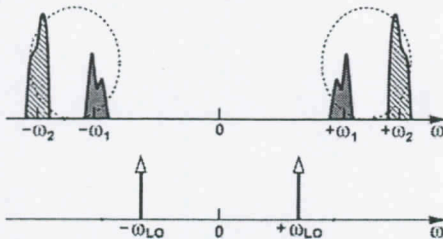


Fig.13

