



Roll No.

ANNA UNIVERSITY (UNIVERSITY DEPARTMENTS)

B.E. / B. Tech / B. Arch (Full Time) - END SEMESTER EXAMINATIONS, APR/MAY 2024

ELECTRICAL AND ELECTRONICS ENGINEERING
VII Semester

EE5701 & Electrical Drives

(Regulations 2019)

Time: 3hrs

Max.Marks: 100

PART- A (10 x 2 = 20 Marks)
(Answer all Questions)

| Q. No | Questions | Marks |
|-------|--|-------|
| 1 | Compare active and passive load torque. | 2 |
| 2 | Write the equation in connection with assessing the stability of an electric drive. . | 2 |
| 3 | What will be the ripple frequency of a single phase full converter and three phase full converter? Assume supply frequency is 60 Hz. | 2 |
| 4 | Define duty cycle in a step up chopper. | 2 |
| 5 | Why stator voltage control scheme employed for induction motor drives with high slip? | 2 |
| 6 | Write the features of current source driven AC drive. | 2 |
| 7 | Define slip power | 2 |
| 8 | Define super synchronous speed. | 2 |
| 9 | What are the benefits of synchronous motor drives? | 2 |
| 10 | Define load commutation. | 2 |

PART- B (5 x 13 = 65 Marks)

| Q. No | Questions | Marks |
|--------|---|-------|
| 11 (a) | Explain the various duty cycles involved in assessing the rating of motors. | 13 |
| 11 (b) | Explain the speed torque conventions involved in the multi-quadrant operation of a motor driving a hoist load. | 13 |
| 12 (a) | Derive the necessary expression for critical speed calculation for single phase full converter fed separately excited DC motor. | 13 |
| OR | | |
| 12 (b) | A 200 V, 875 rpm, 150 A separately excited dc motor has an armature resistance of 0.06Ω . It is fed from a single phase fully-controlled rectifier with an ac source voltage of 220 V, 50 HZ. Assuming continuous conduction, calculate firing angle for rated motor torque and 750 rpm and -500 rpm. | 13 |
| 13 (a) | Discuss the improvement of power factor in a rotor side control of an induction | 13 |

| | | |
|-----------|---|----|
| | motor using necessary diagrams and phasor diagrams | |
| OR | | |
| 13 (b) | Explain the working of three phase AC voltage controller fed three phase induction motor with necessary waveforms. | 13 |
| 14 (a) | Explain self-control of a synchronous motor with necessary diagrams. | 13 |
| OR | | |
| 14 (b) | Explain how V/f control can be implemented in a synchronous motor drive systems | 13 |
| 15 (a) | <p>Design a speed-controlled DC motor drive maintaining the field flux constant. The motor parameters and ratings are as follows</p> <p>220 V ; 8.3 A ; 1470 rpm ; $R_a = 4 \Omega$; $J = 0.0607 \text{ kg-m}^2$; $L_a = 0.072 \text{ H}$; $B_1 = 0.0869 \text{ Nm/rad/sec}$; $K_b = 1.26 \text{ V/rad/sec}$</p> <p>The converter is supplied from 230 V, 3-phase AC at 60 Hz. The converter is linear and its maximum control input voltage is $\pm 10 \text{ V}$. The tachogenerator has the transfer function $G_w(s) = \frac{0.065}{1+0.002s}$. The speed reference voltage has a maximum of 10 V. The maximum current permitted in the motor is 20 A.</p> | 13 |
| 15 (b) | Explain the closed loop operation of DC motor with PID controller. | 13 |

PART- C (1 x 15 = 15 Marks)
(Q.No.16 is compulsory)

| Q. No | Questions | Marks |
|-------|---|-------|
| 16. | <p>A drive has following parameters:</p> <p>$J = 10 \text{ Kg-m}^2$, $T = 100 - 0.1 N$, N-m.</p> <p>Passive load torque $T_l = 0.05 N$, N-m.</p> <p>Where N is the speed in rpm. Initially the drive is operating in steady-state. Now it is to be reversed. For this, motor characteristic is changed to $T = -100 - 0.1N$, N-m. Calculate the time of reversal.</p> | 15 |

