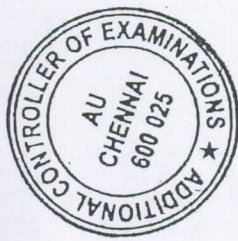


1516124 (FN)



Roll No.

ANNA UNIVERSITY (UNIVERSITY DEPARTMENTS)  
B.E.(FT) END SEMESTER EXAMINATIONS – APRIL/MAY 2024

COMPUTER SCIENCE AND ENGINEERING

EE6351 – Basics of Electrical and Electronics Engineering  
(Regulation 2018 -RUSA)

Time:3 Hours

Max.Marks 100

PART-A (10x2=20 Marks)

(Answer ALL Questions)

| S.No | Questions  | Marks |
|------|--|-------|
| 1.   | Find $v_1$ and $v_2$   | 2     |
|      |  |       |
| 2.   | The delta network consists of balanced resistors of values $R_a=R_b=R_c=R_\Delta=24\Omega$ . Calculate the resistance $R_Y$ for balanced star network.     | 2     |
| 3.   | The turn ratio of transformers is given as 1:2. If the applied voltage in the primary coil is 100 V, then calculate the secondary voltage across the load. | 2     |
| 4.   | What is step angle in stepper motor?   | 2     |
| 5.   | In which region, the BJT is operated as amplifier.   | 2     |
| 6.   | What is voltage divider biasing?   | 2     |
| 7.   | Design an inverting op-amp for a voltage gain of -2.   | 2     |
| 8.   | How an op-amp is operated as integrator and draw the corresponding circuit.  | 2     |
| 9.   | Draw the circuit of 3-bit flash type ADC.  | 2     |
| 10.  | Draw the output characteristics of n-channel MOSFET in depletion type.   | 2     |

**PART -B (8x8=64 marks)**  
**(Answer any 8 questions)**



| S.No | Questions   | Marks |
|------|---|-------|
| 11.  | Explain the operation of Permanent Magnet Moving Coil (PMMC) instrument with appropriate diagram and derive the torque equation.  | 8     |
| 12.  | Calculate the node voltages $i_x$ , $V_1$ and $V_2$ .   | 8     |
|      |   |       |
| 13.  | Calculate the following parameters for the given circuit<br>a. Equivalent impedance $Z_{eq}$ (2 marks)<br>b. Supply current $I$ in polar form (2 marks)<br>c. Real power ( $P$ ) (1 mark)<br>d. Reactive power ( $Q$ ) (1 mark)<br>e. Apparent power ( $S$ ) (1 mark)<br>f. Power factor (1 mark) | 8     |
|      |   |       |
| 14.  | a) Derive the EMF equation of DC machine. (4 marks)<br>b) A 200 V DC shunt motor takes 20 A current while it runs at 800 rpm under full load. The resistance of armature and field windings are 0.25 Ω and 200 Ω respectively. Determine the back EMF. (4 marks)                                  | 8     |

|     |  |   |
|-----|--|---|
| 15. | A single phase transformer has 400 and 800 turns in primary and secondary windings respectively. The net cross-sectional area of the core is $50\text{cm}^2$ and the flux density is $2\text{ Wb/m}^2$ . The primary winding is connected to 50Hz supply at 200 V. Calculate (a) flux in the core (b) transformation ratio (c) emf induced in the secondary winding. | 8 |
| 16. | Why single phase induction machine is not self starting and explain in detail with double field revolving theory. Mention the types of single phase induction motors.  | 8 |
| 17. | a) Explain the characteristics and the operation of PN junction diode under (i) unbiased (ii) forward biased (iii) reverse biased condition with suitable diagrams. (6 marks)<br><br>b) What is avalanche breakdown and Zener breakdown? (2 marks)   | 8 |
| 18. | Find the minimum and maximum value of $R_L$ to maintain a constant load voltage in the given circuit. The input voltage is $V_i=20\text{V}$ , $R_s=222\Omega$ , maximum power allowed in Zener diode is $P_{z(\text{max})}=0.4\text{ W}$ .   | 8 |
|     |  |   |
| 19. | Explain the characteristics of any two types of negative feedback amplifier with neat sketch   | 8 |
| 20. | Derive the expression for summing operational amplifier circuit in inverting and non-inverting configuration.  | 8 |
| 21. | Briefly explain the operation of binary weighed Digital to Analog converter (DAC) with necessary diagram.  | 8 |
| 22. | Explain in detail the construction and working of n-channel MOSFET in depletion and enhancement mode of operation  | 8 |



**PART-C (2x8=16 marks)**

ANSWER ALL THE QUESTIONS
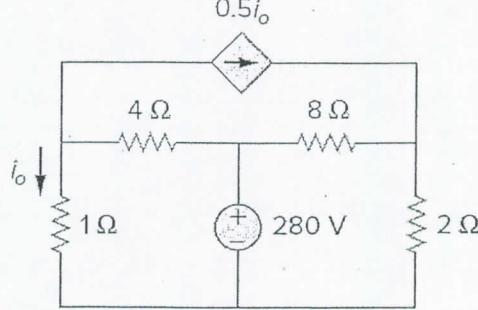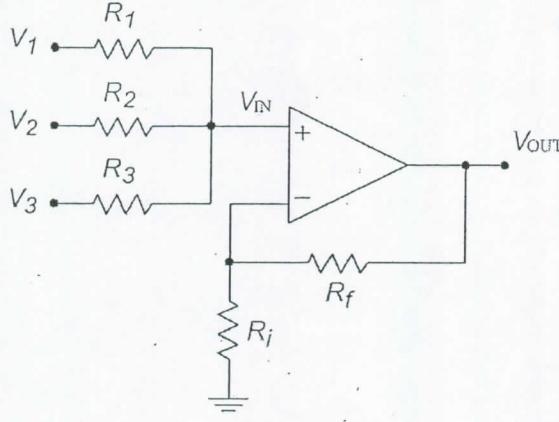
| S.No | Questions   | Marks |
|------|---|-------|
| 23.  | <p>Find the mesh currents and <math>i_o</math> in the given circuit.</p>    | 8     |
| 24.  | <p>Calculate output voltage <math>V_{out}</math> for the given circuit where <math>R_1=1\Omega</math>, <math>R_2=2\Omega</math>, <math>R_3=4\Omega</math>, <math>R_f=4\Omega</math>, <math>R_i=1\Omega</math>, <math>V_1=1V</math>, <math>V_2=3V</math>, <math>V_3=5V</math>.</p>  | 8     |

